

International Symposium on Physical Design



Design and Optimization of Quantum Electronic Circuits

Giovanni De Micheli

EPFL



What is cool out there?


▲ Making chips faster by cooling them

- ▽ CryoCMOS

- ▽ Superconducting single-quantum gates

- ▽ Quantum computing

 ▲ We set the operating conditions to beat the RC



Superconducting electronics

Classical computing

High operational speed

Dataflows operate in the 50-100 GHz range

Gates require clocking to operate

Pipelined logic has to be balanced

Refrigeration (4 K) energy offsets power efficiency

Refrigeration technology is slowly improving

020]

Quantum computing technologies

QC leverages superposition and entanglement
Support algorithms with lower complexity


A wide array of realization technologies
Superconductors, silicon, optics

Scaling and noise are still issues
Qubit count and coherence time are limited

Refrigeration to tenth of mK for noise reasons
Interfacing to host is complex


Superconductors and JJs

- ▲ A superconductor is a material where
 - ▽ *Resistivity* vanishes and *magnetic flux* field is expelled
 - ▽ When below a *critical temperature* T_c
- ▲ *Josephson junction* - JJ
 - ▽ Superconducting wire interrupted by thin insulator
 - ▽ Nb/ AlO_x /Nb or Al/ AlO_x /Al
- ▲ *Supercurrent* $I_s = I_c \sin(\phi)$, where ϕ is the phase difference of electrodes wave functions
- ▲ *Critical current*: I_c – max current in SC state

 

Some history

 
- ▲ IBM ran a large SCE program until 1983
 - ▽ The project failed because of the *latching* issue
- ▲ Several Japanese companies followed IBM's path
 - ▽ They improved the *materials* but still had latching issues




- ▲ I_b is slightly below I_c
- ▲ I_{in} makes the JJ be resistive
- ▲ A fast voltage transition 0 $\rightarrow$ 1
- ▲ More difficult to reset JJ -- latching
- ▲ Slower transition 1 $\rightarrow$ 0

Some history - *Single-flux quantum* SFQ

 - ▲ Likharev radically changed to *pulse-based* signalling
 - ▽ *Single-flux quantum* logic SFQ
 - ▽ Input is short pulse $\int V(t)dt = \phi_0 = h/2e = 2.07 \text{ mv ps}$
 - ▽ Load is *overdamped*
 - ▽ An output pulse is generated




Josephson transmission line

 


Fanout and Splitters

▲ Output pulse has fanout equal to 1



▽ Splitter circuit – splitter trees

 

The S/R latch or SQUID

 

  - ▲ Two persistent states
 - ▽ Corresponding to direction of current in loop J1 – L1 - J2
 - ▽ Flux quantum
- ▲ Input sets to 1 – Clock resets to 0





Principles of combinational cells



- ▲ Signal encoding: 1 = pulse -- 0 = no pulse
- ▲ Cell has two stable states:
 - ▽ Direction of current flow in a loop

- ▲ Operation

  
- ▽ Inputs are evaluated when clock is present
- ▽ Output is issued at end of clock
- ▽ Clock resets the state



Example of OR and AND

  


 Combinational cells are more complex than registers




[Likharev – Stony Brook]


The SFQ variants

 

Achievements

 

 47 GHz SFQ FFT Processor [Ke et al.,2021]




2.5 GHz 4-bit RISC [Ayala et al.,2021]

Achievements

Synopsys SuperTools Superconducting Electronics Phase 2A Program

First Fully Automated Superconducting Microcontroller Design Demonstration with Fusion Compiler

 The First Fully-Automated ERSFQ Microcontroller Circuit including CTS, Splitter Insertion, Power Delivery and PTL Routing – all desired features for SCE Technology automation



Fully synthesized AMD 2901 [Amaru et al., 2021]

Some ballpark numbers

Logic	Clock Freq. [GHz]	$E_{\text{bit}} / I_c \Phi_0$	Typical I_c [mA]	EDP [aJ·ps]
CMOS	4	-	-	$\sim 10^5$
RSFQ [1]	50	19	150	120
eSFQ [2]	20	0.8	150	12
RQL [3]	10	0.33	150	10
LV-RSFQ [4]	20	3.5	150	54
AQFP [5]	5	0.0083	50	0.086
Quantum limit	-	-	-	5.3×10^{-5}

[1] X. Peng et al., IEICE Trans. Electron. **E97.C**, 188 (2014).

[2] M. H. Volkmann et al., Supercond. Sci. Technol. **26**, 015002 (2013).


[3] Q. P. Herr et al., J. Appl. Phys. **109**, 103903 (2011).

[4] M. Tanaka et al., IEEE Trans. Appl. Supercond. **23**, 1701104 (2013).

[5] N. Takeuchi et al., Supercond. Sci. Technol. **28**, 015003 (2015).

AQFP -- Adiabatic quantum flux parametron

- ▲ Input is a current
- ▲ Direction of current encodes 1/0
- ▲ Circuit has two loops
 - ▽ Either one is conducting – state 1/0
- ▲ Input evaluated when clock is present
 - ▽ May force a gradual transition of conducting loop
 - ▽ Creates a corresponding output signal

 

[Goto 56]

[Yoshikawa, Ayala et al. Yokohama National University]

AQFP buffer and derivatives

▲ Buffer

- ▽ Output follows input

▲ Inverter


- ▽ Buffer where output coil is reversed

▲ Majority gate


- ▽ Three buffers in parallel with an inductive coupler

▲ Extensions:

 - ▽ Logic gates NPN-equivalent to majority
- ▽ AND-2 and OR-2 by creating “constant buffers”



Adiabatic Quantum Flux Parametron (AQFP)

 

Logic design principles

▲ Balancing:

- ▽ When considering a logic network graph, all paths from inputs to any node have same *length*

▲ Fanout:


- ▽ All multiple fanout points need signal *splitting*

▲ Logic optimization:

- ▽ Logic should be optimized by *majority logic*, especially when majority is native abstraction

Path balancing for SFQ

 ▲ Assumption: splitters are not clocked in SFQ



[Katam, Pedram, TAS18]


Dynamic programming for SFQ

- ▲ Assumption: splitters are not clocked in SFQ
- ▲ PBMap (based on AIG representation in ABC)
 - ▽ Given a node and its cuts
 - ▽ Best local solution minimizes the sum of cost of the *children nodes* plus cost of the *inserted buffers*
 - ▽ Proceed bottom up
- ▲ For tree topologies gives optimum solution
- ▲ For DAGs, it is a heuristic
 - ▽ Area-retiming can refine solution

[Pasandi, Pedram, ICCAD 19]

Splitter insertion for AQFP

 - ▲ A splitter is a clocked buffer with a passive fork
 - ▽ Inserting splitters imbalances a circuit
 - ▽ Require additional buffers




[Cai et al., ICCD 19]

Majority logic synthesis



 - ▽ Exploit redundancy of majority function
- ▽ Boolean substitution



What is in for physical design ?

- ▲ A new set of interesting problems
 - ▽ Inductors are the limit in placement
- ▲ Wiring can be done by *passive or Josephson* transmission lines
 - ▽ Relatively less critical for speed (compared to CMOS)
- ▲ Clock routing is complicated
 - ▽ Because of reaching out to all gates
- ▲ Adiabatic realizations are even more complex
 - ▽ Power and clock routing

Conclusions

- ▲ There is strong evidence that SCE circuits can provide us with:
 - ▽ Faster computing
 - ▽ Higher energy-efficient computation
- ▲ Current limitations are:
 - ▽ Scalability to larger realizations
 - ▽ Lack of EDA design tools and open libraries
 - ▽ Cooling systems
- ▲ The technical difficulties are surmountable and new opportunities are in reach

Thank you



FONDS NATIONAL SUISSE
SCHWEIZERISCHER NATIONALFONDS
FONDO NAZIONALE SVIZZERO
SWISS NATIONAL SCIENCE FOUNDATION

SYNOPSIS[®]



Warm congratulations to Ricardo Reis

▲ Recipient of the Lifetime Achievement Award

